

Johns Hopkins Engineering

Module 1: Boolean & Digital Logic

EN605.204 Computer Organization



JOHNS HOPKINS
WHITING SCHOOL
of ENGINEERING

Introduction

- How do bits change/flow through digital circuits?
- What is Boolean logic?
- How do digital circuits implement Boolean logic?

What is a “bit”?

- Computer circuits are based on Boolean algebra
- Boolean algebra operates on 1's and 0's
- Claude Shannon showed the relationship between Boolean algebra and digital circuits in 1930's

Logical NOT

- Takes in a single bit as input and negates ("flips") it
- Can be denoted using the \sim or \neg character

Input (X)	Output ($\neg X$)
0	1
1	0

Logical OR

- Takes two bits as input and outputs a 1 if either input was a 1
- Can be denoted using the \vee , \cup , or $+$ character

Input (X, Y)		Output ($X \vee Y$)
0	0	0
0	1	1
1	0	1
1	1	1

Logical AND

- Takes two bits as input and outputs a 1 if both inputs were 1
- Can be denoted using the \wedge , \cap , or $*$ character

Input (X, Y)		Output ($X \wedge Y$)
0	0	0
0	1	0
1	0	0
1	1	1

Logical XOR

- Two bits as input and outputs a 1 if exactly one input was a 1
- Can be denoted using the \otimes character

Input (X, Y)		Output ($X \otimes Y$)
0	0	0
0	1	1
1	0	1
1	1	0

Logical NOR

- Two bits as input and outputs a 1 if no inputs were a 1


Input (X, Y)		Output $\neg(X \vee Y)$
0	0	1
0	1	0
1	0	0
1	1	0

Logical NAND

- Two bits as input and outputs a 1 if at least 1 bit was a 0


Input (X, Y)		Output $\neg(X \wedge Y)$
0	0	1
0	1	1
1	0	1
1	1	0

Logic Gates

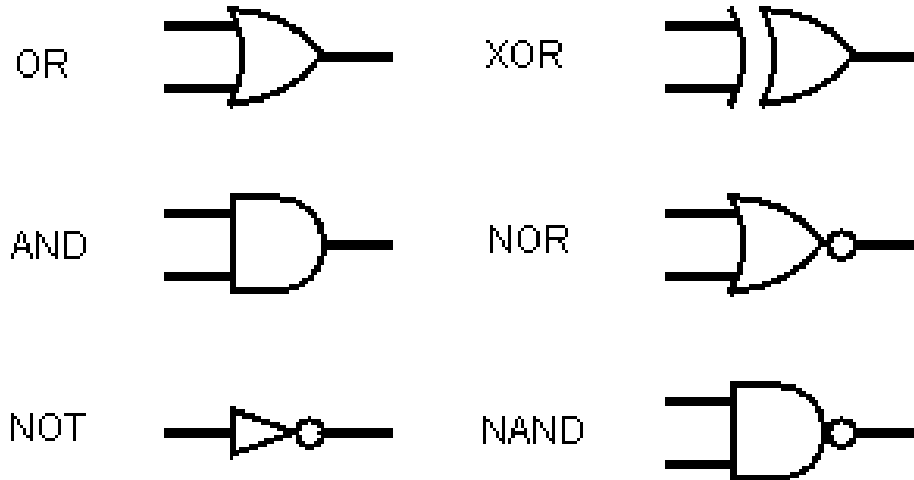


Combinational Logic

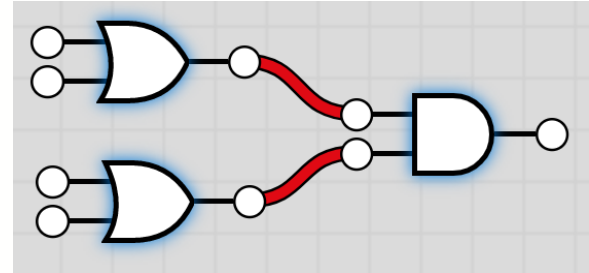- Computer logic is implemented using physical "gates"
- Gates can be strung together to build more complex logic
- Example: $\text{AND}(\text{OR}(W, X), \text{OR}(Y, Z))$
 - Input: $\{0, 0, 0, 1\}$
 - $= \text{AND}(\text{OR}(0, 0), \text{OR}(0, 1))$
 - $= \text{AND}(0, 1)$
 - $= 0$



Universal Logic Gates

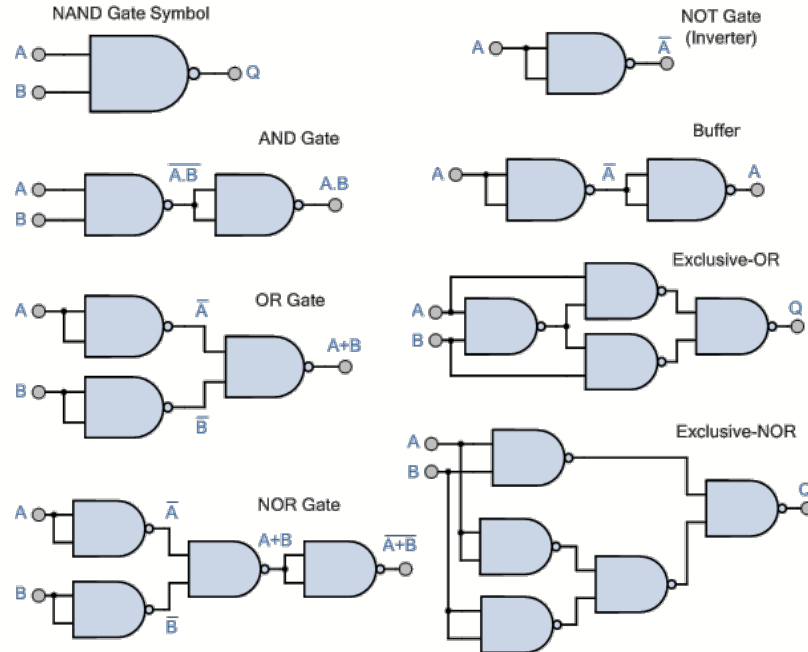- NOR and NAND gates are "universal"; they can simulate any logical operation



Laws of Boolean Logic

Input (X, Y)	Output $\neg(X \wedge Y)$	
Identity	$X \wedge 1 = X$	$X \vee 0 = X$
Complementation	$X \wedge \neg X = 0$	$X \vee \neg X = 1$
Double Negation	$\neg(\neg X) = X$	
Idempotent	$X \wedge X = X$	$X \vee X = X$
Dominance	$X \wedge 0 = 0$	$X \vee 1 = 1$
Commutative	$X \wedge Y = Y \wedge X$	
Associative	$X \wedge Y \wedge Z = X \wedge (Y \wedge Z) = (X \wedge Y) \wedge Z$	
Distributive	$X \wedge (Y \vee Z) = (X \wedge Y) \vee (X \wedge Z)$ $X \vee (Y \wedge Z) = (X \vee Y) \wedge (X \vee Z)$	

DeMorgan's Law

- $(X \text{ OR } Y)$ and $(X \text{ AND } Y)$ are called "propositions"
- $\neg(X \text{ OR } Y) = \neg X \text{ AND } \neg Y$
 - The proposition $X \text{ OR } Y$ fails if X and Y are false
 - Ex: "I don't like the Cowboys (X) or Patriots (Y)" = "I don't like the Cowboys (X) and I don't like the Patriots (Y)."
- $\neg(X \text{ AND } Y) = \neg X \text{ OR } \neg Y$
 - The proposition fails if either X is false or Y is false
 - Ex: "I don't want a sandwich unless it has both ham (X) and cheese (Y)."